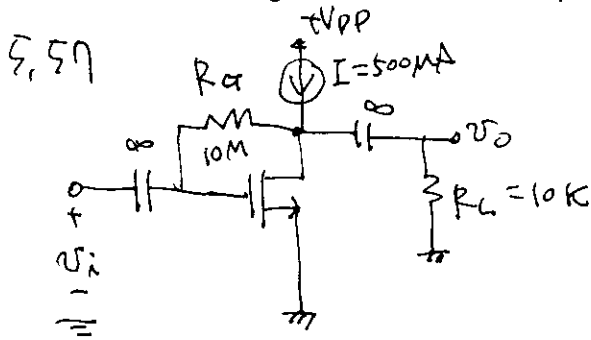


HW#8 Solution (Prob. sets)



$$V_D = 2V, |V_t| = 0.9, V_A = 50V$$

$$\text{Voltage gain } \frac{v_o}{v_i} = -g_m \cdot (r_o \parallel R_L)$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2 \cdot I_D}{V_{GS} - V_{TH}}$$

In this circuit, $V_D = V_G = 2V$ ($\because I_G = 0$ so no voltage drop across R_G)

$$\Rightarrow g_m = \frac{2 \cdot 500 \mu A}{2 - 0.9} = 9.09 \times 10^{-4} \text{ (A/V)}$$

$$r_o = \frac{V_A}{I_D} = 100 k\Omega, (r_o \parallel R_L) = 9.09 k\Omega$$

$$\therefore \frac{v_o}{v_i} = -8.2645$$

If I increased to $1mA$, consider

$$I_D = K \cdot (V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_A}\right)$$

For $I_D = 500 \mu A$, $V_{GS} = 2$, we can find K .

$$\therefore K = \frac{I_D}{(V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_A}\right)} = \frac{500 \mu A}{(2 - 0.9)^2 \left(1 + \frac{2}{50}\right)} = 3.97 \times 10^{-4} \text{ (A/V}^2\text{)}$$

Hence, for $I_D = 1mA$, new $V_D = V_D'$ is

$$\Rightarrow 1mA \approx K (V_D' - V_t)^2 \text{ (ignored } V_A \text{ term for simplicity)}$$


$$\Rightarrow V_D = 2.48$$

with $V_D = 2.48$ & $I_D = 1mA$, by following same way to find the gain,

$$A_V = -10.5057$$

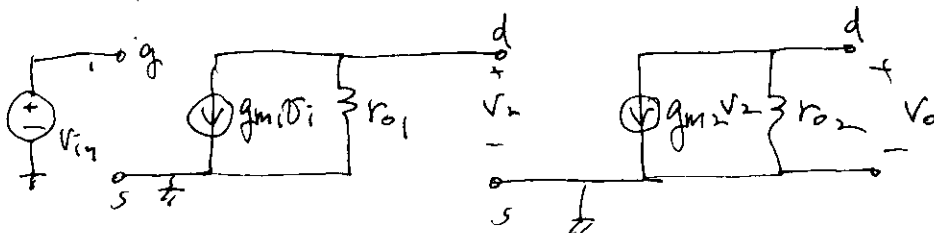5.75 small-signal model


notice that small signal model for NMOS & PMOS are ^{the} same.




$$\frac{v_2}{v_i} = -g_{m1} r_{o1}, \quad \frac{v_0}{v_2} = -g_{m2} r_{o2}$$

$$\therefore A_V = \frac{v_0}{v_i} = (g_{m1} r_{o1})(g_{m2} r_{o2})$$

5.81

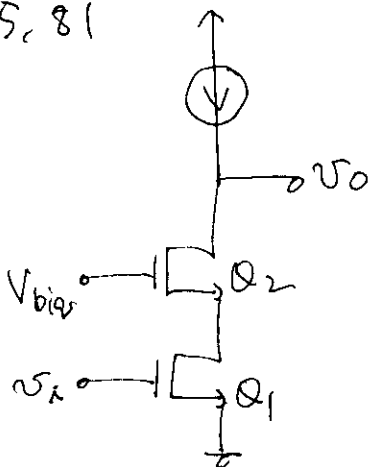

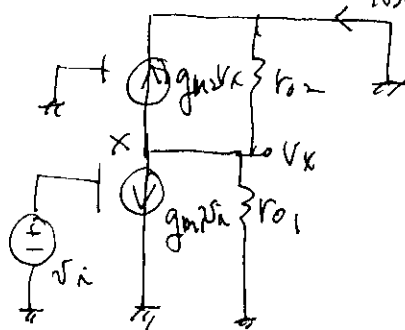a) short-circuit transconductance $\triangleq \frac{i_{short}}{v_i} = G_{m,short}$



$$\rightarrow i_{short} = -\frac{v_X}{r_{o2}} - g_{m2} v_X = -(g_{m2} + \frac{1}{r_{o2}}) v_X \quad \text{--- ①}$$

$$\rightarrow \text{KCL at } X: g_{m1} v_i + \frac{v_X}{r_{o1}} + \frac{v_X}{r_{o2}} + g_{m2} v_X = 0$$

$$\Rightarrow v_X = \frac{-g_{m1} v_i}{(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m2})} \quad \text{--- ②}$$


combining ① & ② gives

$$i_{short} = (g_{m2} + \frac{1}{r_{o2}}) \cdot \frac{1}{(g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}})} g_{m1} v_i$$

$$\approx g_{m1} v_i \quad (\because \frac{1}{r_{o1}} \approx 0)$$

$$\therefore \boxed{\frac{i_{short}}{v_i} = g_{m1}}$$

(b)

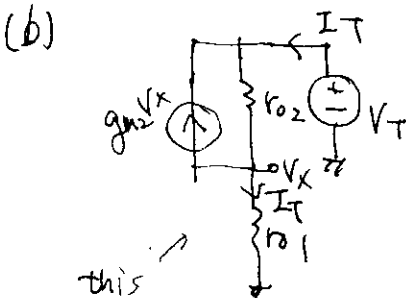

this current source is removed because $V_{gs1}=0$

$$\Rightarrow V_T = (I_T + g_{m2}V_X)r_{o2} + I_T \cdot r_{o1}$$

$$V_X = I_T \cdot r_{o1}$$

$$\Rightarrow V_T = I_T (g_{m2}r_{o1}r_{o2} + r_{o1} + r_{o2})$$

$$\therefore R_{out} = g_{m2}r_{o1}r_{o2} + r_{o1} + r_{o2}$$

(c)

$$\frac{v_o}{v_i} = G_{in,short} \cdot R_{out} \approx g_{m1} (g_{m2}r_{o1}r_{o2})$$

$$\text{Without } Q_2, \frac{v_o}{v_i} = g_{m1}r_{o1}$$


Therefore, gain is boosted by the factor of $g_{m2}r_{o1}$

2, 8

| | $\frac{v_o}{v_i}$ | R_{in} |
|-----|-------------------------------|-------------|
| (a) | $-\frac{100}{10} = -10$ | $10k\Omega$ |
| (b) | $-\frac{100}{10} = -10$ | $10k\Omega$ |
| (c) | $-\frac{100}{10} = -10$ | $10k\Omega$ |
| (d) | $-\frac{100}{10} = -10$ | $10k\Omega$ |
| (e) | $0 (= -\frac{0}{10})$ | $10k\Omega$ |
| (f) | $-\infty (= -\frac{100k}{0})$ | 0Ω |

2.16

(a)

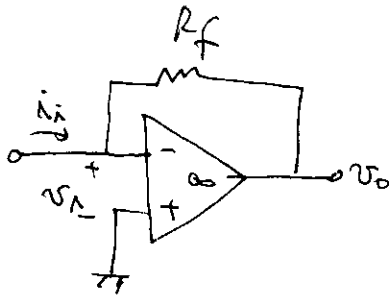

For $A = \infty$,

$v_- = 0$ ($\because v_- = v_+$ if $A = \infty$)


Hence,

$$i_{in} = \frac{0 - v_o}{R_f} \Rightarrow R_m = \frac{v_o}{i_{in}} = -R_f$$

$$R_{in} = \frac{v_{in}}{i_{in}} = 0$$

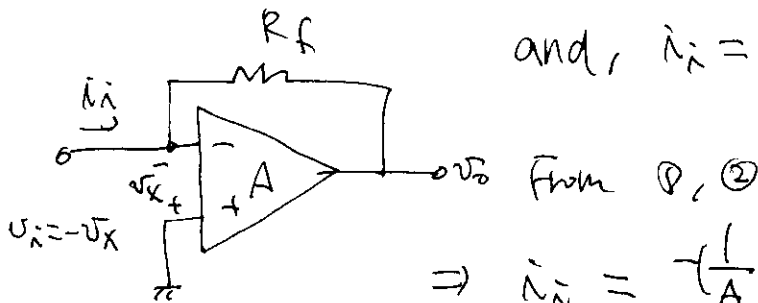(b) if gain is finite, $v_o = A \cdot v_x \dots (1)$

$$\text{and, } i_{in} = \frac{-v_x - v_o}{R_f} \dots (2)$$



$$\Rightarrow i_{in} = \frac{\left(\frac{1}{A} + 1\right)v_o}{R_f}$$


$$\therefore R_m = \frac{v_o}{i_{in}} = - \frac{R_f}{1 + \frac{1}{A}}$$

$$R_{in} = \frac{v_{in}}{i_{in}}, \quad i_{in} = \frac{-v_x - A v_x}{R_f} = \frac{(1+A)}{R_f} \cdot v_x$$

$$\therefore R_{in} = \frac{R_f}{1+A}$$

Aspice solution.

1.

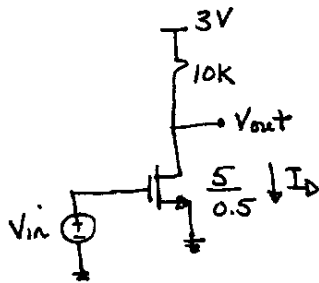

$$V_{out} = 3 - 10K \cdot I_D \quad (1)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_t)^2 \quad (2)$$

at the edge of saturation, $V_{out} = V_{in} - V_t$

$$\Rightarrow V_{in} - V_t = 3 - 10K I_D = 3 - 10^4 \cdot \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_t)^2$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 \times 8.85 \times 10^{-12} \text{ F/m}}{10^{-7} \text{ m}} = 345.2 \times 10^{-6} \text{ F/m}^2$$

$$\mu_n = 600 \frac{\text{cm}^2}{\text{Vs}} \quad (\text{From Spice model})$$

$$\Rightarrow \mu_n C_{ox} = 600 \times 10^{-4} \times 345.2 \times 10^{-6} = 20.7 \times 10^{-6} \text{ A/V}^2$$

$$V_{in} - V_t = 3 - 10^4 \times \frac{1}{2} \times 20.7 \times 10^{-6} \times 10 (V_{in} - V_t)^2$$

$$\Rightarrow V_{in} - V_t = 1.29 \quad ; \quad V_t = 0.7 \quad (\text{from SPICE model})$$

$$\Rightarrow \boxed{V_{in} = 1.99 \text{ V}}$$

This is very close to the simulated value.

In simulation, the intersection of V_{out} & $V_{in} - V_t$ occurs at $V_{in} = 1.99 \text{ V}$

*Common-Source MOS Amplifier Circuit

2

** Circuit Description **

* Power Supplies

Vdd Vdd 0 DC 3V

Vss Vss 0 DC 0V

* Input Voltage

Vin in 0 DC 0V AC 1V

* Common-Source Circuit

* MOS D G S B

M0 out in Vss Vss nch L=0.5u W=5u

Rd Vdd out 10k

* Model Definitions

* TOX = Oxide thickness in Meters

* U0 = Surface mobility in cm²/Vs

* VTO = Zero-bias threshold voltage in V

* LAMBDA = channel-length modulation in 1/V

* CBD = base-drain junction capacitance

* CBS = base-source junction capacitance

.model nch nmos (LEVEL=1 TOX=1e-7 U0=600 +VTO=0.7 LAMBDA=0.02 CBD=20fF
+CBS=20fF)

** Analysis Request **

* DC Analysis (SOURCE START STOP INCREMENT)

.dc Vin 0V 3V 5mV

** Output Request **

.probe


.end

^
Date/Time run: 12/04/02 14:37:42

*Common-Source MOS Amplifier Circuit

Temperature: 27.0

(A) hw7 (active)

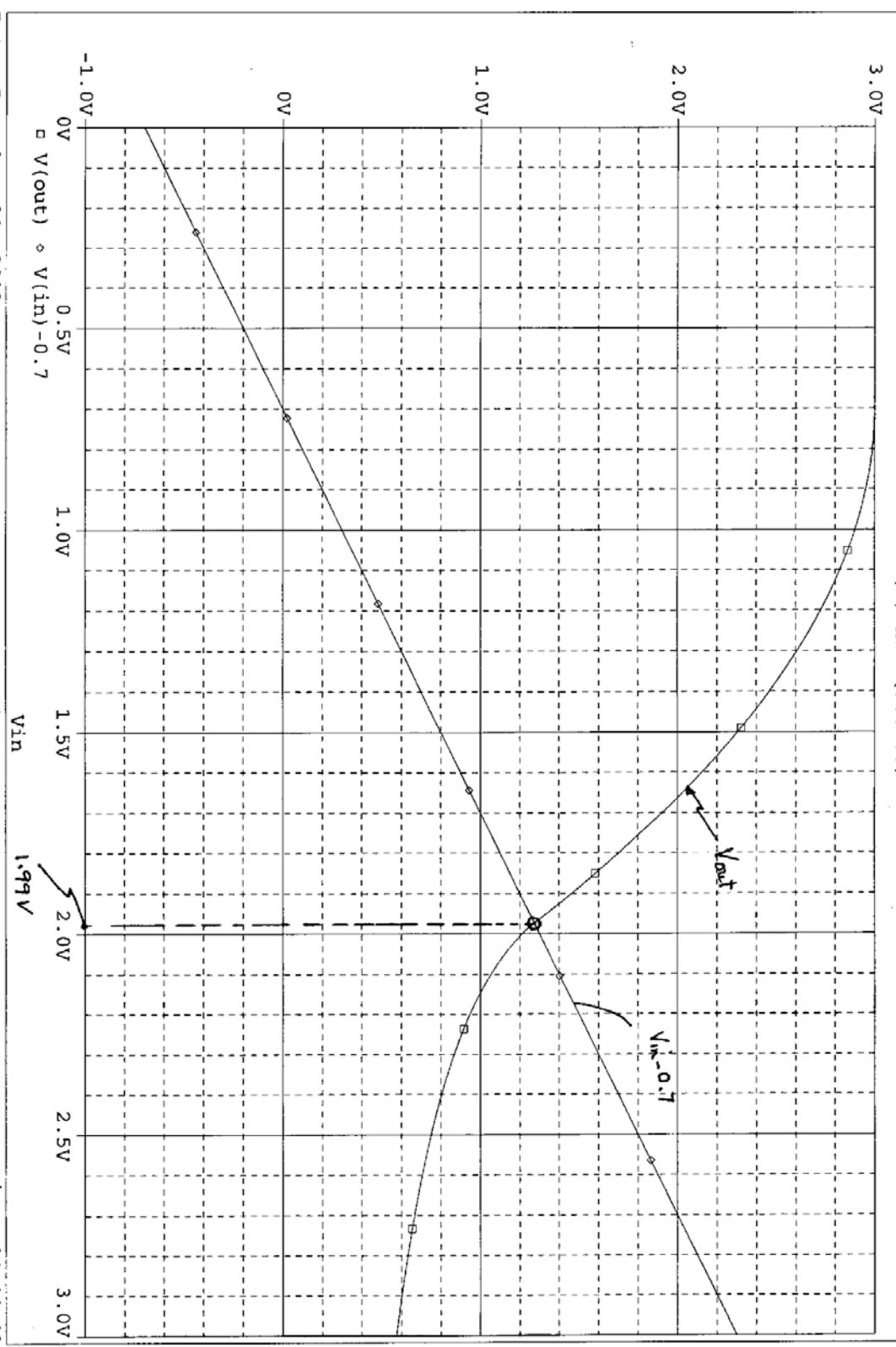

Date: December 04, 2002

Page 1

Time: 14:44:49