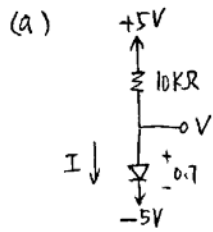


HW #3 solution

①


3.59



Using constant-voltage-drop model ($V_D = 0.7V$)

$$V = -5V + 0.7V = -4.3V$$

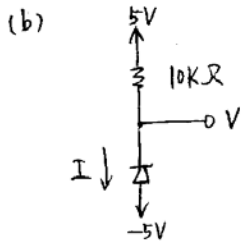
$$I = \frac{5 - (-4.3)}{10K} = 0.93 \text{ mA}$$



Diode is off


$$I = 0$$

$$V = 5V$$

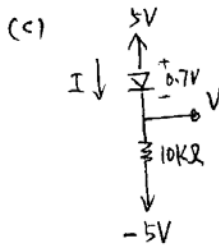

$$V = 5 - 0.7 = 4.3V$$

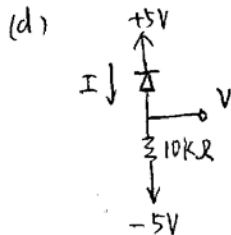
$$I = \frac{4.3 - (-5)}{10K} = 0.93 \text{ mA}$$



Diode is off

$$I = 0$$

$$V = -5V$$

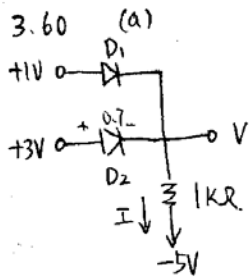


D_1 off
 D_2 on

$$\Rightarrow V = 3 - 0.7 = 2.3V$$

$$I = \frac{2.3V - (-5V)}{1k\Omega} = 7.3mA$$

(2)

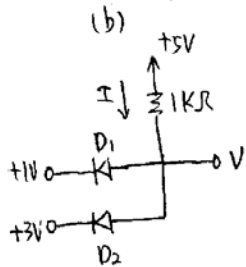


D_2 off
 D_1 on

$$V = 1.7V$$

$$I = \frac{5V - 1.7V}{1k\Omega} = 3.3mA$$


3.61 (a)

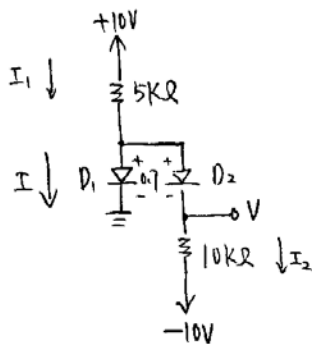

D_1, D_2 both on

$$\Rightarrow V = 0$$
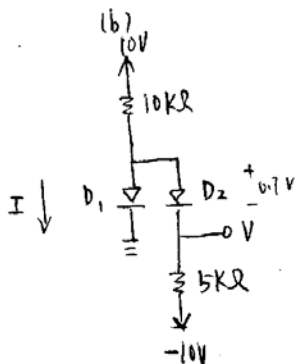
$$I = I_1 - I_2 = \frac{10 - 0.7}{5k\Omega} - \frac{0 - (-10)}{10k\Omega} = 0.86mA$$





D_1 off
 D_2 on

$$\Rightarrow I = 0$$

$$\Rightarrow V = \frac{10V - (-10V) - 0.7V}{10k\Omega + 5k\Omega} \cdot 5k\Omega + (-10V)$$

$$= -3.55V$$

3.62 (a)

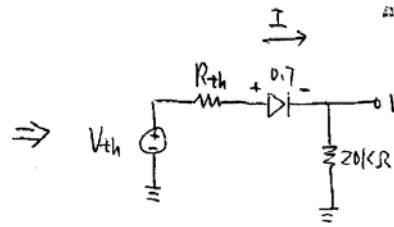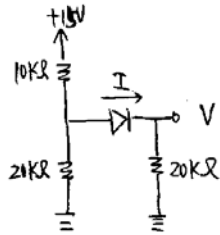



$$V_{th} = \frac{20k\Omega}{10k\Omega + 20k\Omega} \cdot 15V = 10V$$

$$R_{th} = 10k\Omega // 20k\Omega = 6.67k\Omega$$

$$V = \frac{V_{th} - 0.7}{R_{th} + 20k\Omega} \cdot 20k\Omega = 7V$$

$$I = \frac{V_{th} - 0.7}{R_{th} + 20k\Omega} = 0.35mA$$

(b)

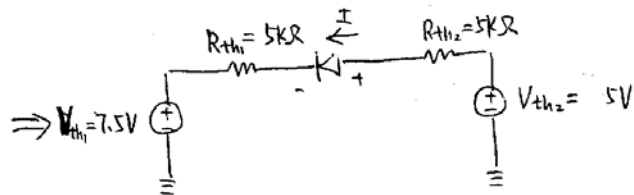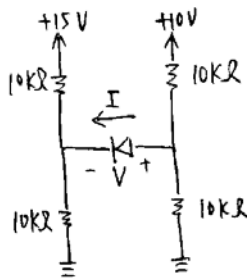


Diode is off

$$I = 0$$

$$V = 5V - 7.5V = -2.5V$$

3.65

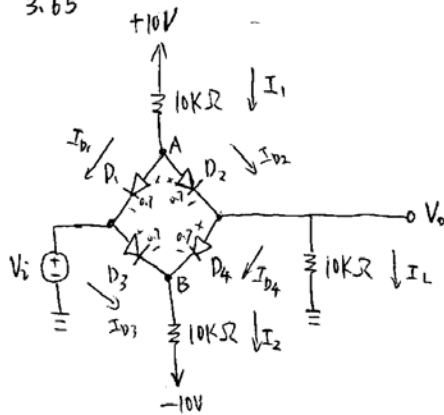① For V_i close to zero D_1, D_2, D_3 & D_4 are on $V_o = V_i$ (As long as all four diodes on)

$$I_1 = \frac{10 - V_i - 0.7}{10k\Omega} = \frac{9.3 - V_i}{10k\Omega}$$

$$I_2 = \frac{10 + V_i - 0.7}{10k\Omega} = \frac{9.3 + V_i}{10k\Omega}$$

$$I_L = \frac{V_i}{10k\Omega}$$

As V_i increases in the positive direction, I_1 decreases & I_L increasesNote that $I_1 > I_{D_2}$ for D_1, D_2 both on and $I_{D_2} > I_L$ for D_2, D_4 both on


$$\Rightarrow I_1 > I_{D_2} > I_L$$

Now as I_L increases and I_1 decreases, a value for V_i will be reached at which this condition is no longer satisfied. This boundary is reached when $I_1 = I_{D_2} = I_L$. At this point, D_1, D_4 turn off

$$I_1 = \frac{9.3 - V_i}{10k\Omega} = \frac{V_i}{10k\Omega} = I_L$$


$$\Rightarrow V_i = 4.65 \text{ V}$$

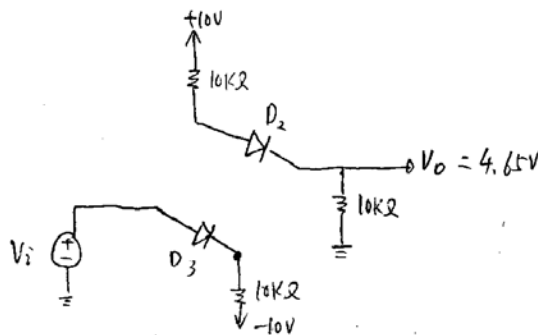For $V_i \geq 4.65 \text{ V}$, D_1, D_4 off and D_2, D_3 on. and the original circuit is reduced to



observe that V_o remains constant at $4.65V$ for $V_i \geq 4.65V$ (5)

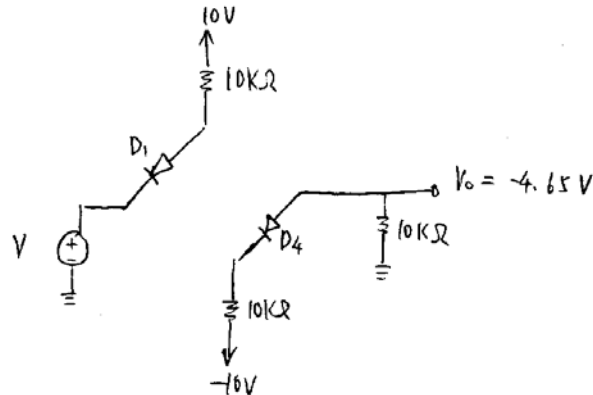The symmetry of the circuit indicates that a similar limiting situation occurs at a negative value of V_i . Specifically, for $V_i \leq -4.65$, D_2, D_3 off and D_1, D_4 on, the circuit reduces to



observe that V_o remains constant at $-4.65V$. In conclusion, the given circuit provides :

$$V_o = V_i, \quad -4.65 \leq V_i \leq 4.65$$

$$V_o = 4.65V, \quad V_i \geq 4.65V$$

$$V_o = -4.65V, \quad V_i \leq -4.65V$$