

Chapter 8

Exercise 8.18

The expressions for the flip-flop inputs are

$$T_A = Q_A + Q'_B$$

$$T_B = Q_A + Q_B$$

The flip-flops change state in every clock pulse depending only on the previous state. The transition table is

PS $Q_A(t)Q_B(t)$	FF inputs $T_A(t) \quad T_B(t)$		NS $Q_A(t+1)Q_B(t+1)$
00	1	0	10
01	0	1	00
10	1	1	01
11	1	1	00

Let us define the following encoding:

Q_AQ_B	
00	S_0
01	S_2
10	S_1
11	S_3

The resulting state table is

PS	NS
S_0	S_1
S_1	S_2
S_2	S_0
S_3	S_0

The state diagram is presented in Figure ???. It is an autonomous modulo-3 counter.

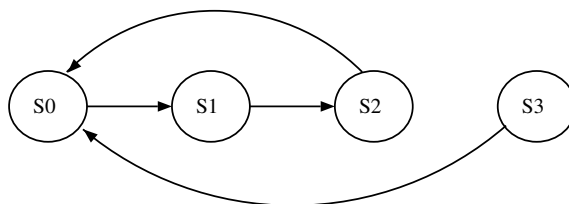


Figure 8.1: State diagram for Exercise 8.18

Exercise 8.20

The expressions for the flip-flop inputs are:

$$T_A = Q_A + Q_B$$

$$T_B = Q'_A + Q_B$$

The transition table is

PS $Q_A(t)Q_B(t)$	FF inputs $T_A(t)T_B(t)$	NS $Q_A(t+1)Q_B(t+1)$
00	01	01
01	11	10
10	10	00
11	11	00

Let us define the following encoding:

Q_AQ_B	
00	S_0
01	S_1
10	S_2
11	S_3

The resulting state table is

PS	NS
S_0	S_1
S_1	S_2
S_2	S_0
S_3	S_0

The state diagram is shown in Figure ???. The network implements an autonomous modulo-3 counter.

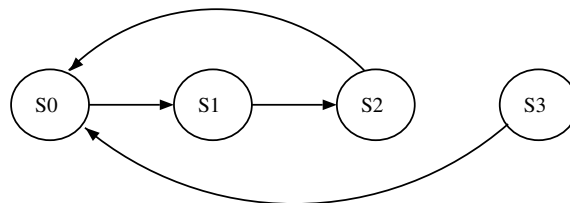


Figure 8.2: State diagram for Exercise 8.20

Exercise 8.24

Since the output at time t depends on the inputs at time $t-3, t-2, t-1$, it is necessary to store these in the state register. That is, the register consists of three flip-flops such that

$$Q_2(t) = x(t-3)$$

$$Q_1(t) = x(t-2)$$

$$Q_0(t) = x(t-1)$$

Consequently, the state description is

$$Q_2(t+1) = Q_1(t)$$

$$Q_1(t+1) = Q_0(t)$$

$$Q_0(t) = x(t)$$

$$z = x(t-3) \oplus x(t-2) \oplus x(t-1) \oplus x(t) = Q_2 \oplus Q_1 \oplus Q_0 \oplus x$$

If we use D flip-flops, we get

$$D_2 = Q_1$$

$$D_1 = Q_0$$

$$D_0 = x$$

The sequential network is shown in Figure ??.

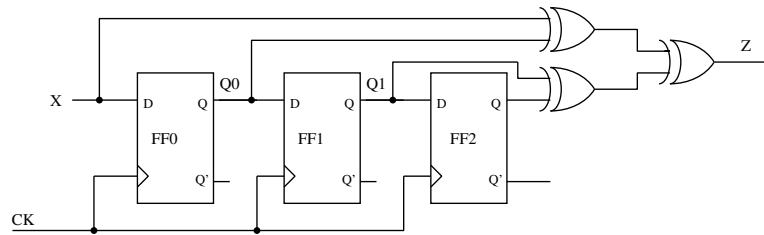


Figure 8.3: Network for Exercise 8.24

Exercise 8.26

The state corresponds to the count. That is,

$$s(t+1) = (s(t) + 1) \bmod 3$$

Using a radix-2 representation for the count we get the following state table

PS Q_2Q_1	Input	
	$x = 0$	$x = 1$
00	00	01
01	01	10
10	10	00
	NS	

Since the excitation function of a *SR* flip-flop is

PS	NS	
	0	1
0	0-	10
1	01	-0
	SR	

we get the following switching expressions

$$S_2 = xQ_1 \qquad S_1 = xQ_2'Q_1'$$

$$R_2 = xQ_2 \qquad R_1 = xQ_1$$

The output is obtained directly from the state register. The sequential network is shown in Figure ??.

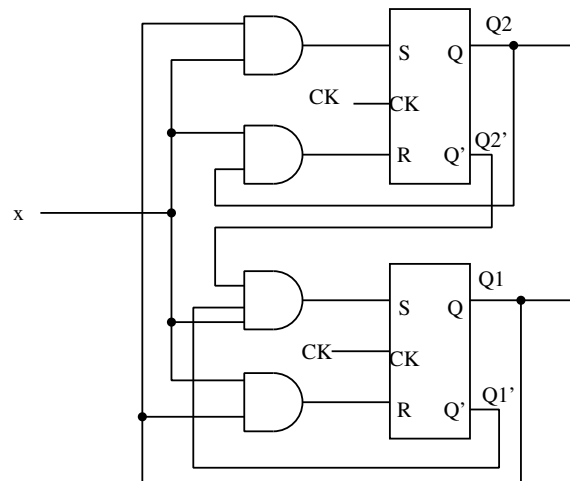


Figure 8.4: Network for Exercise 8.26

Exercise 8.32 Modulo-3 binary counter using “one flip-flop per state” approach.

The counter has 3 states $S \in \{0, 1, 2\}$, thus 3 flip-flops are required. The state codes are:

$y_2y_1y_0$	State
0 0 1	0
0 1 0	1
1 0 0	2

The counter changes state when the input $x = 1$. The state diagram for the counter is shown in Figure ???. The switching expressions for the network can be obtained by inspection of the state diagram:

$$Y_2 = S_1x + S_2x' = y_1x + y_2x'$$

$$Y_1 = y_0x + y_1x'$$

$$Y_0 = y_2x + y_0x'$$

$$z_1 = y_2$$

$$z_0 = y_1$$

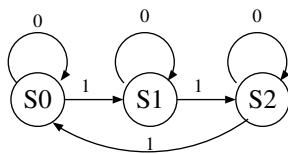


Figure 8.5: State Diagram for a Modulo-3 Counter

The corresponding network is shown in Figure ??.

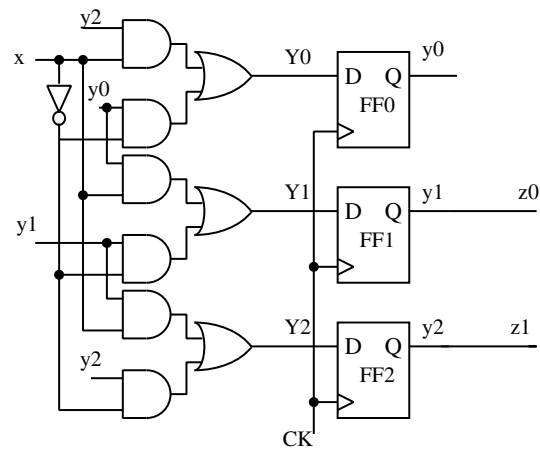


Figure 8.6: Modulo-3 counter - Exercise 8.32