

Chapter 8

Exercise 8.6:

The pattern generator for the sequence *abcaba* is described by the following transition table:

PS	NS/ <i>z</i>
A	B/ <i>a</i>
B	C/ <i>b</i>
C	D/ <i>c</i>
D	E/ <i>a</i>
E	F/ <i>b</i>
F	A/ <i>a</i>

Let us define the following encoding:

$y_2y_1y_0$	State	z_1z_0	
000	A	00	a
001	B	01	b
010	C	10	c
011	D		
100	E		
101	F		

From the state table and the previous encoding we get the following table and K-maps:

PS	NS/ z_1z_0
000	001/00
001	010/01
010	011/10
011	100/00
100	101/01
101	000/00
101	- - -/- -
101	- - -/- -

Y_2 :	$ \begin{array}{c} \overline{y_0} \\ \begin{array}{ c c c c } \hline 0 & 0 & 1 & 0 \\ \hline 1 & 0 & - & - \\ \hline \end{array} \end{array} $	Y_1 :	$ \begin{array}{c} \overline{y_0} \\ \begin{array}{ c c c c } \hline 0 & 1 & 0 & 1 \\ \hline 0 & 0 & - & - \\ \hline \end{array} \end{array} $	Y_0 :	$ \begin{array}{c} \overline{y_0} \\ \begin{array}{ c c c c } \hline 1 & 0 & 0 & 1 \\ \hline 1 & 0 & - & - \\ \hline \end{array} \end{array} $
z_1 :	$ \begin{array}{c} \overline{y_0} \\ \begin{array}{ c c c c } \hline 0 & 0 & 0 & 1 \\ \hline 0 & 0 & - & - \\ \hline \end{array} \end{array} $	z_0 :	$ \begin{array}{c} \overline{y_0} \\ \begin{array}{ c c c c } \hline 0 & 1 & 0 & 0 \\ \hline 1 & 0 & - & - \\ \hline \end{array} \end{array} $		

The expressions we get from the K-maps are:

$$\begin{aligned} Y_2 &= y_1 y_0 + y_2 y_0' \\ Y_1 &= y_2' y_1' y_0 + y_1 y_0' \\ Y_0 &= y_0' \\ z_1 &= y_1 y_0' \\ z_0 &= y_2' y_1' y_0 + y_2 y_0' \end{aligned}$$

The network that implements a canonical version of this sequential network is presented in Figure ?? on page ??.

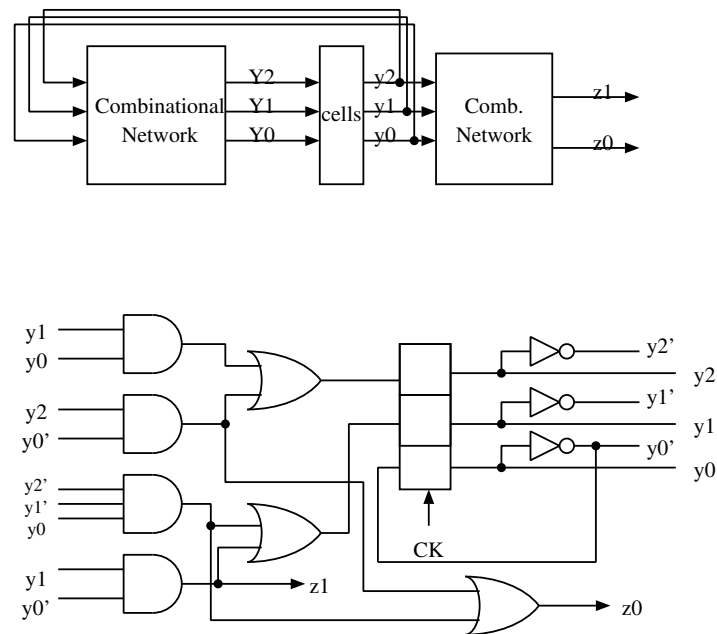



Figure 8.1: Pattern generator of Exercise 8.6

Exercise 8.8

We need a 3-bit vector to represent the six states and a 2-bit vector to represent the output. Let us define the following encoding:

$y_2y_1y_0$	State	z_1z_0	
000	A	00	a
001	B	01	b
010	C	10	c
011	D		
100	E		
101	F		

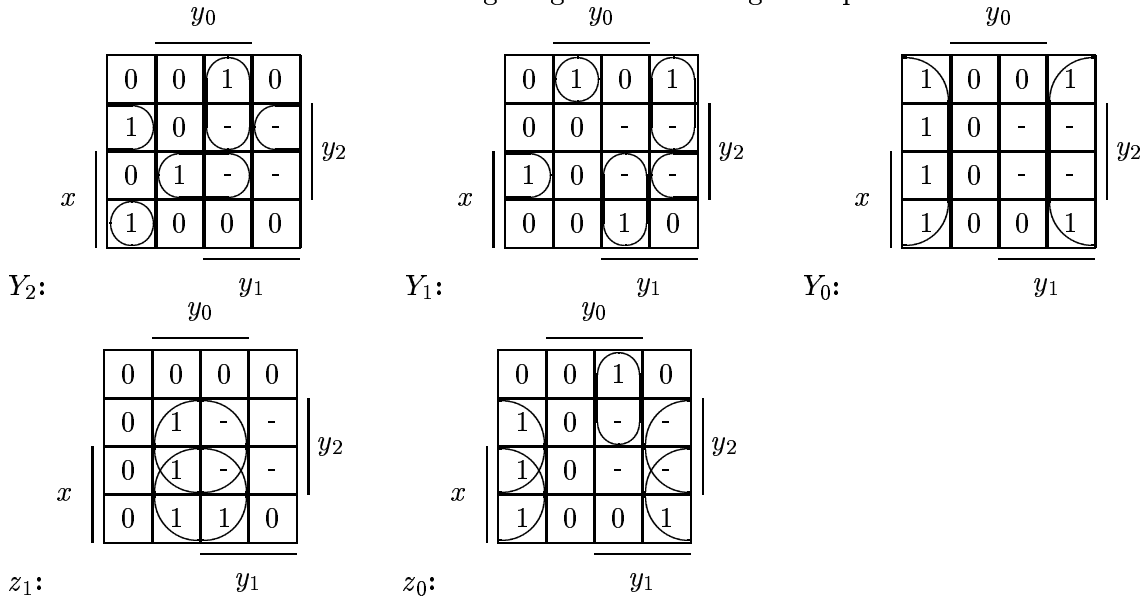From the state table and the encoding we get the following K-maps.



The corresponding switching expressions are

$$Y_0 = y'_0$$

$$Y_1 = x'y'_2y'_1y_0 + x'y_1y'_0 + xy_2y'_0 + xy_1y_0$$

$$Y_2 = x'y_2y'_0 + x'y_1y_0 + xy_2y_0 + xy'_2y'_1y'_0$$

$$z_1 = y_2y_0 + xy_0$$

$$z_0 = x'y_1y_0 + y_2y'_0 + xy'_0$$

The sequential network is shown in Figure ?? on page ??.

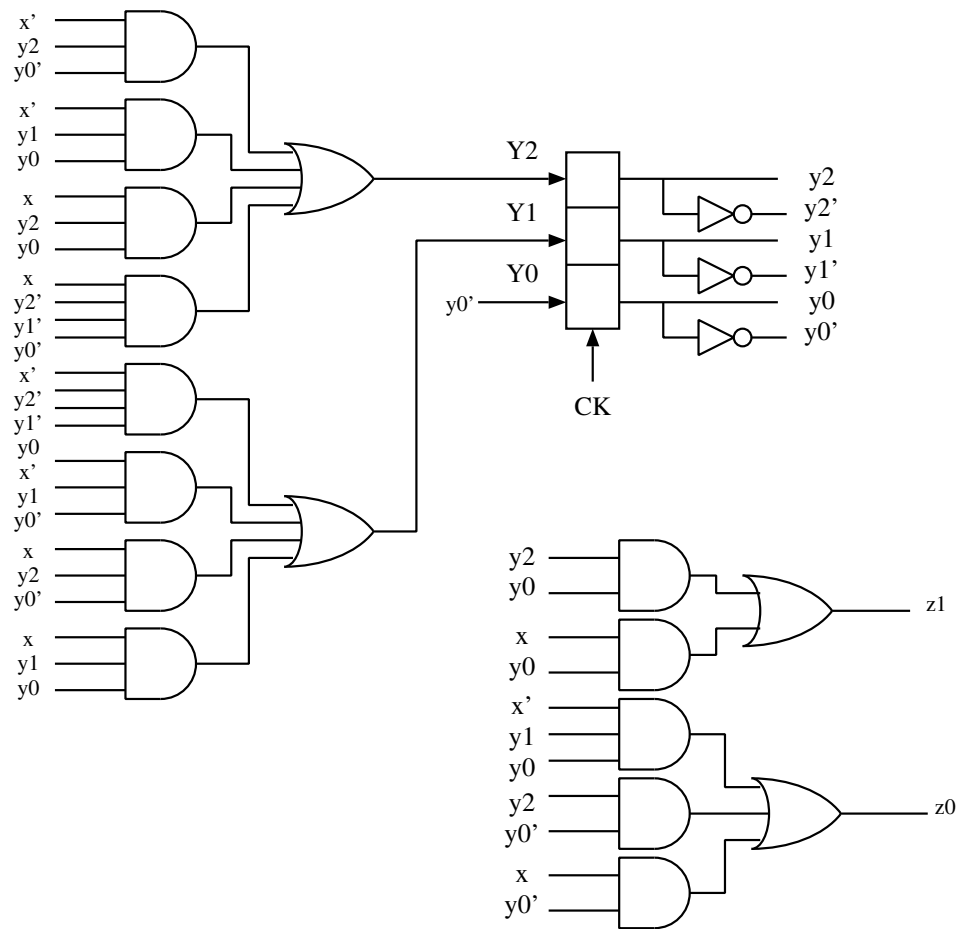


Figure 8.2: Sequential network for Exercise 8.8

Exercise 8.16 From the network we obtain the following table, based on the expressions below:

$$J_A = K_A = xQ_B$$

$$J_B = K_B = x$$

PS $Q_A Q_B$	Input		Input	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
00	0000	0011	00	01
01	0000	1111	01	10
10	0000	0011	10	11
11	0000	1111	11	00
	$J_A K_A J_B K_B$		NS	

The outputs are expressed as:

$$z_3 = Q_A Q_B$$

$$z_2 = Q_A Q'_B$$

$$z_1 = Q'_A Q_B$$

$$z_0 = Q'_A Q'_B$$

Giving the following names to the states:

State Name	Code
S_0	00
S_1	01
S_2	10
S_3	11

we get the transition table:

PS $Q_A Q_B$	Input		Output
	$x = 0$	$x = 1$	
S_0	S_0	S_1	0
S_1	S_1	S_2	1
S_2	S_2	S_3	2
S_3	S_3	S_0	3
	NS		

The state diagram for the given network is presented in Figure ??, and corresponds to a modulo-4 counter with decoded output.

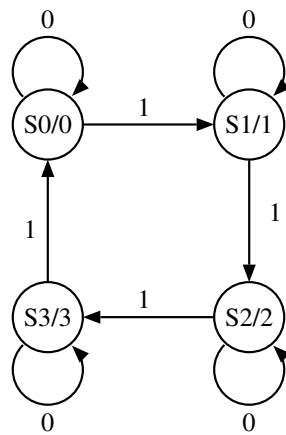


Figure 8.3: State diagram for Exercise 8.16