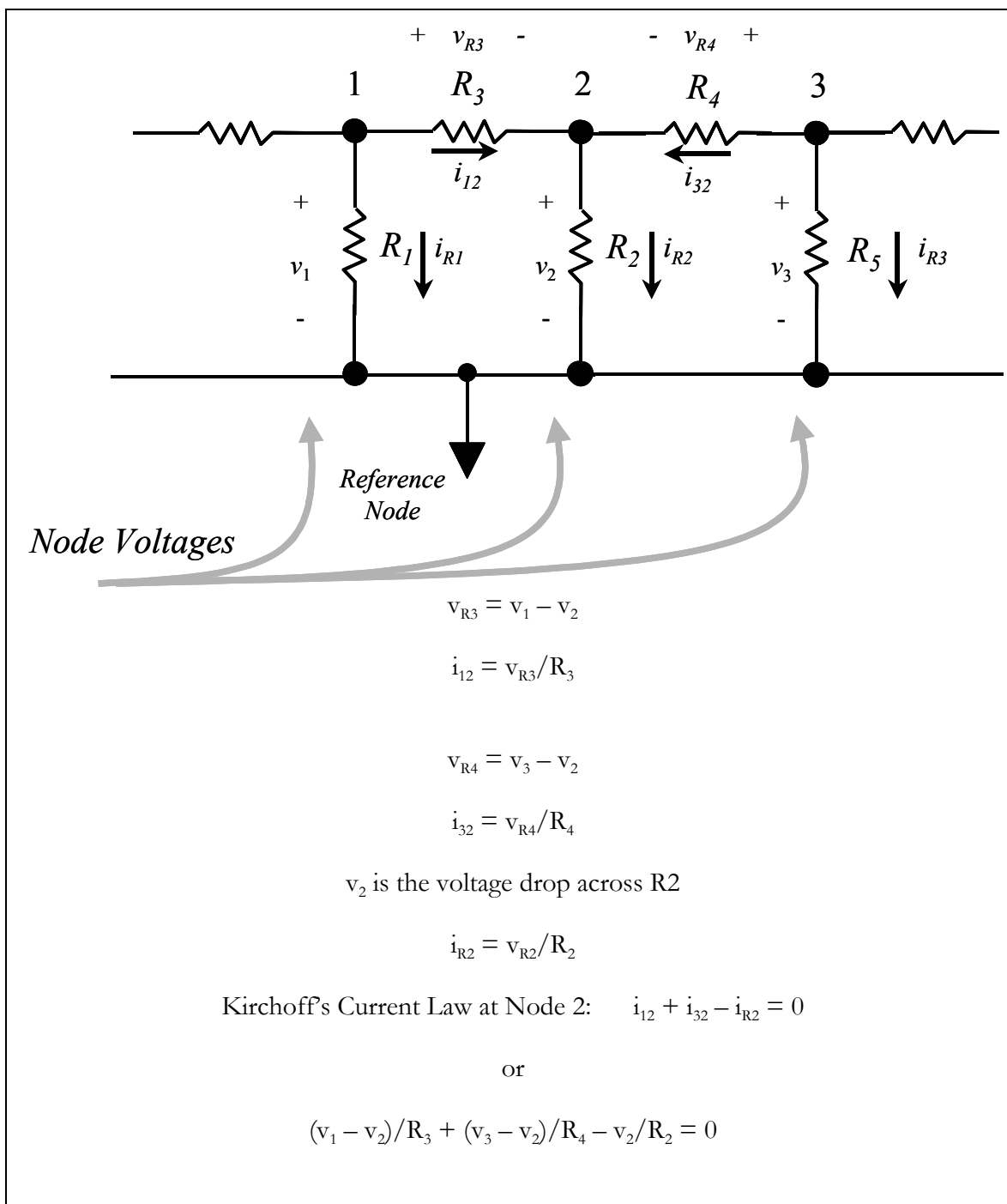

Tutorial: Typical Circuit Structures and Corresponding Node Voltage Equations

For this Tutorial, we will consider the problem of constructing the node voltage equations using Kirchoff's Current Law for virtually *all* the common forms of sources and resistors combinations that may appear between nodes.

We will form node voltage equations at Essential Nodes (where, by definition, three or more elements share a node).

What elements can exist between Essential circuit nodes:

- 1) Case 1: One resistor (or one resistor equivalent). (If resistors appear in series or parallel between Essential Nodes, then they will be replaced by one resistor equivalent).
 - a. This resistor can be connected between two Essential Nodes (see Page 2)
 - b. or, between an Essential Node and the Reference Node (see Page 2)
 - c. Please note the procedure for constructing the Node Voltage Equations.
- 2) Case 2: One Voltage Source between an Essential Node and the Reference Node with two polarities(see Page 8)
 - a. This eliminates the need for one Node Voltage Equation – since the Node Voltage is known.
 - b. Please note the procedure for constructing the Node Voltage Equations.
 - c. The Node Voltage equation at the node to which the source is connected is simply that this node voltage equals the source voltage !
- 3) Case 3: One resistor (or one resistor equivalent) and one Voltage Source
 - a. This combination can be connected between two Essential Nodes with two polarities (see Page 4 and 5)
 - b. or, between an Essential Node and the Reference Node with two polarities (equivalent to the circuits on Page 3)
 - c. Please note the procedure for constructing the Node Voltage Equations.
- 4) Case 4: One Voltage Source
 - a. This combination can be connected between two Essential Nodes with two polarities (see Page 6)
 - b. This can be solved directly or via a Super Node (see Page 7)
 - c. **Please note the constraint condition.**
- 5) Case 5: One Current Source with or without an additional series resistor.
 - a. This can be connected between two Essential Nodes, or
 - b. Or, between an Essential Node and the Reference.
 - c. Here, we simply incorporate the current source value into our KCL equation evaluated at each node to which the current source is connected.
 - d. (As we have explained, this cannot be replaced by a Supernode. A Supernode is a construct applied only in the event of a voltage source where the node voltage difference does not explicitly determine current flow, as is the case for resistors.).



The Node Voltage Equation at Node 2 is simply:

$$v_2 = V_{S1}$$

Also,

$$i_{12} = v_{R3}/R_3$$


$$v_{R4} = v_3 - v_2 = v_3 - V_{S1}$$

$$i_{32} = v_{R4}/R_4$$

Kirchoff's Current Law at Node 3: $-i_{32} - i_{34} - i_{R5} = 0$

or

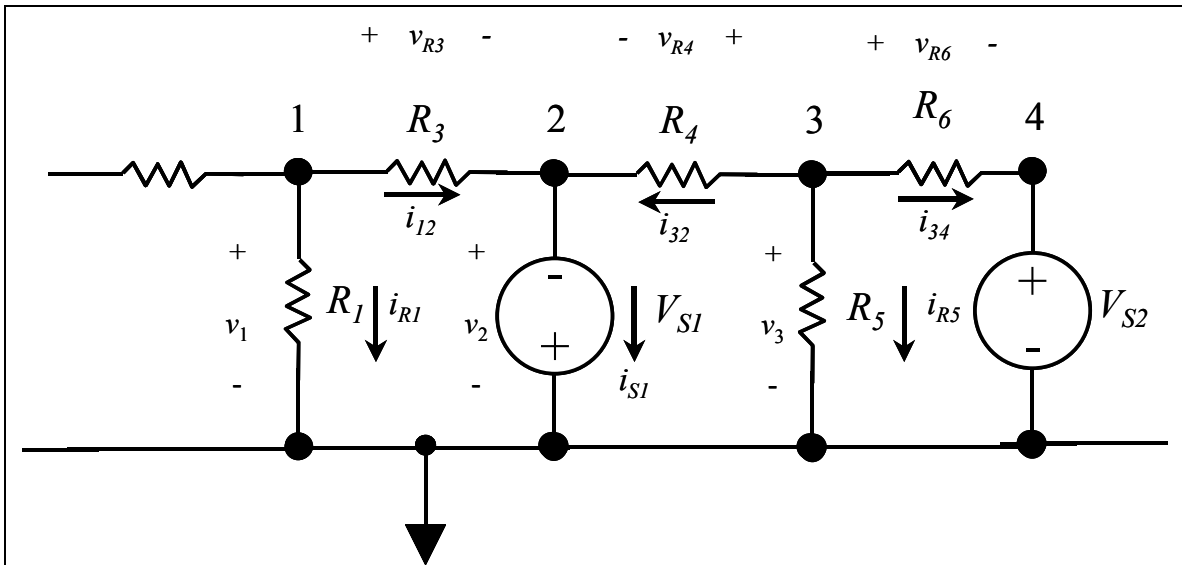Node Voltage Equation at Node 3: $-(v_3 - V_{S1})/R_4 - (v_3 - V_{S2})/R_6 - v_3/R_5 = 0$



The Node Voltage Equation at Node 2 is simply:

$$v_2 = -V_{S1}$$

Also,

$$i_{12} = v_{R3}/R_3$$


$$v_{R4} = v_3 - v_2 = v_3 + V_{S1}$$

$$i_{32} = v_{R4}/R_4$$

$$\text{Kirchoff's Current Law at Node 3: } -i_{32} - i_{34} - i_{R5} = 0$$

or
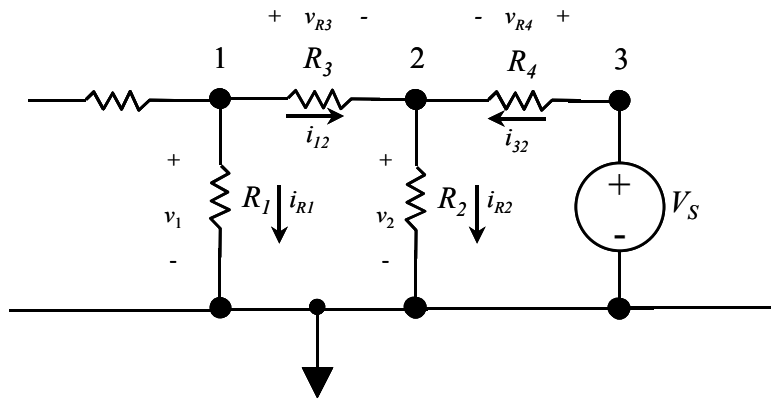
$$\text{Node Voltage Equation at Node 3: } -(v_3 + V_{S1})/R_4 - (v_3 - V_{S2})/R_6 - v_3/R_5 = 0$$



Consider the Essential Node, 2.

$$v_{R4} = v_3 - v_2 = V_S - v_2$$

$$i_{32} = v_{R4}/R_4$$


v_2 is the voltage drop across R_2

$$i_{R2} = v_{R2}/R_2$$

$$\text{Kirchoff's Current Law at Node 2: } i_{12} + i_{32} - i_{R2} = 0$$

or
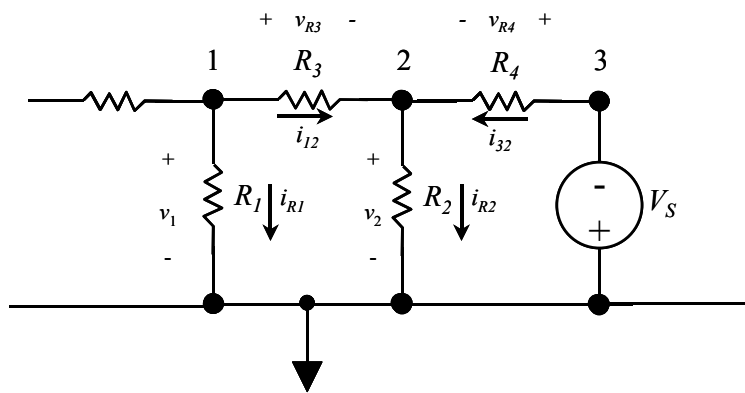
$$(v_1 - v_2)/R_3 + (V_S - v_2)/R_4 - v_2/R_2 = 0$$




Considering a reversed polarity for the voltage source:

$$\text{Kirchoff's Current Law at Node 2: } i_{12} + i_{32} - i_{R2} = 0$$

or
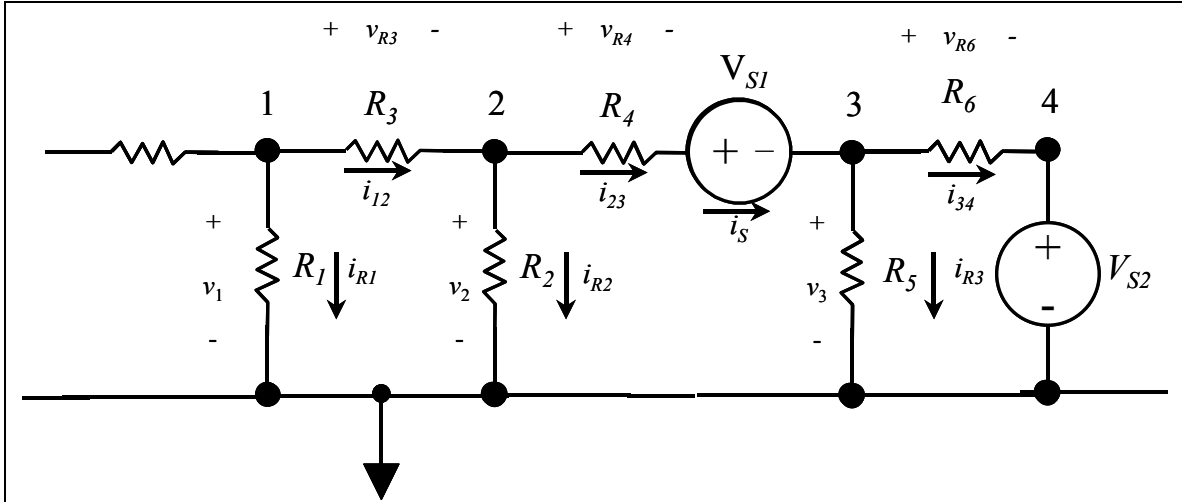
$$(v_1 - v_2)/R_3 + (-V_S - v_2)/R_4 - v_2/R_2 = 0$$



$$v_{R3} = v_1 - v_2$$

$$i_{12} = v_{R3}/R_3$$

Solve for v_{R4} to obtain i_{23} via Ohm's Law. Find this via KVL. KVL involving a loop from Reference to Node 2 to Node 3 and back to Reference:

$$v_2 - v_{R4} - V_{S1} - v_3 = 0$$

So,

$$v_{R4} = v_2 - v_3 - V_{S1}$$

$$\text{Now, } i_{23} = v_{R4}/R_4$$


Also, v_2 is the voltage drop across R_2

$$\text{So, } i_{R2} = v_{R2}/R_2$$

$$\text{Kirchoff's Current Law at Node 2: } i_{12} - i_{23} - i_{R2} = 0$$

or
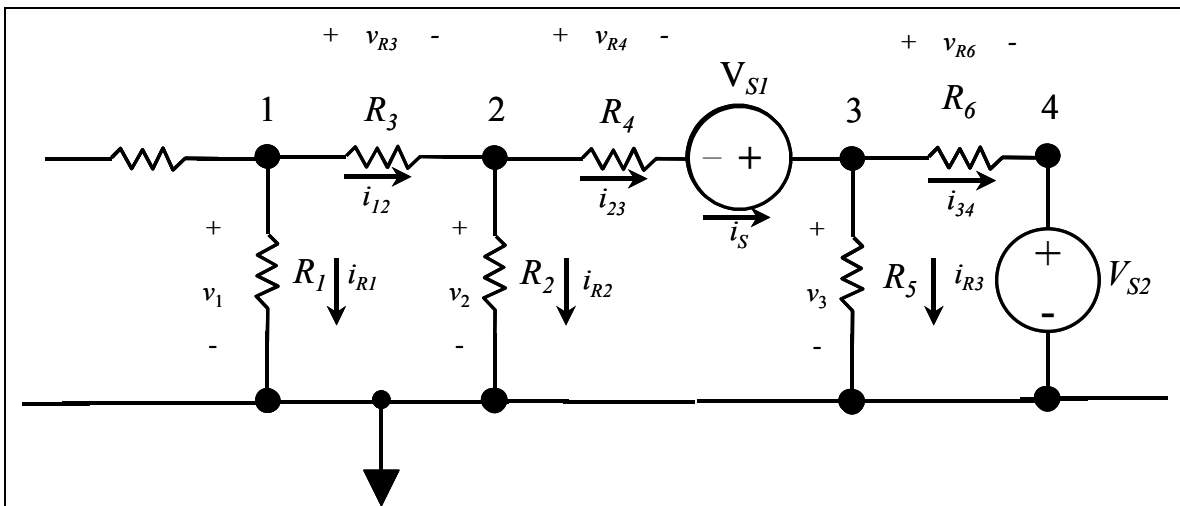
$$(v_1 - v_2)/R_3 - (v_2 - v_3 - V_{S1})/R_4 - v_2/R_2 = 0$$



Now, reversing polarity of the voltage source between nodes 2 and 3 with respect to the previous circuit.

$$v_{R3} = v_1 - v_2$$

$$i_{12} = v_{R3}/R_3$$

Solve for V_{R4} to obtain i_{23} via Ohm's Law. Find this via KVL!. KVL involving a loop from Reference to Node 2 to Node 3 and back to Reference:

$$v_2 - v_{R4} + V_{S1} - v_3 = 0$$

So,

$$v_{R4} = v_2 - v_3 + V_{S1}$$

$$\text{Now, } i_{23} = v_{R4}/R_4$$


Also, v_2 is the voltage drop across R_2

$$\text{So, } i_{R2} = v_{R2}/R_2$$

$$\text{Kirchoff's Current Law at Node 2: } i_{12} - i_{23} - i_{R2} = 0$$

or
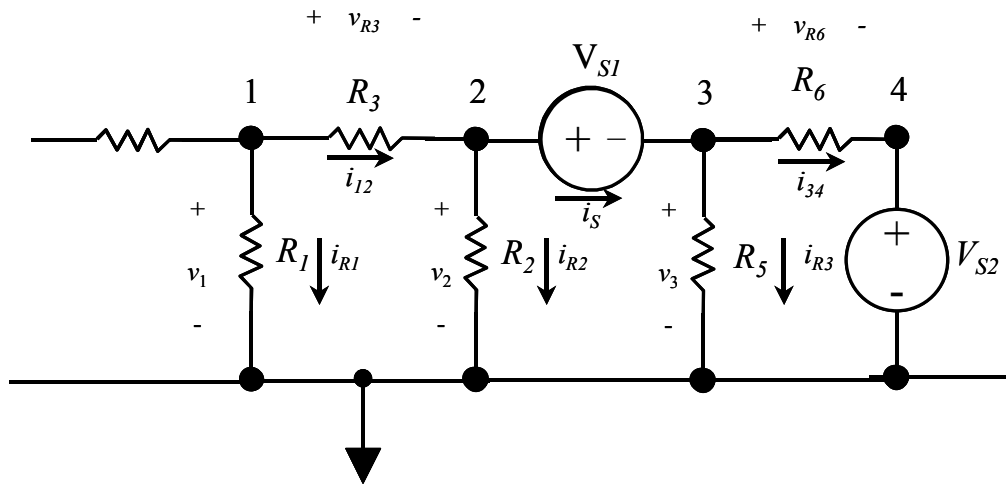
$$(v_1 - v_2)/R_3 - (v_2 - v_3 + V_{S1})/R_4 - v_2/R_2 = 0$$



Kirchoff's Current Law at Node 2: $i_{12} - i_s - i_{R2} = 0$

or

$$(v_1 - v_2)/R_3 - i_s - v_2/R_2 = 0$$

Kirchoff's Current Law at Node 3: $i_s - i_{34} - i_{R3} = 0$

or

$$i_s - (v_3 - V_{S2})/R_6 - v_3/R_5 = 0$$

combining we have:


$$(v_1 - v_2)/R_3 - v_2/R_2 - (v_3 - V_{S2})/R_6 - v_3/R_5 = 0$$

Now, we are apparently missing information at this point. If the branch 2-3 was occupied by a resistor, then Ohm's Law would provide a condition on the voltage drop v_{23} . This would have provided enough information to solve for current and voltage values. But, the voltage source produces V_s *independent* of its current. We thus have no local condition that we can immediately write down relating this current and voltage.

But, we have a constraint condition!

$$v_2 - v_3 = V_{S1}$$

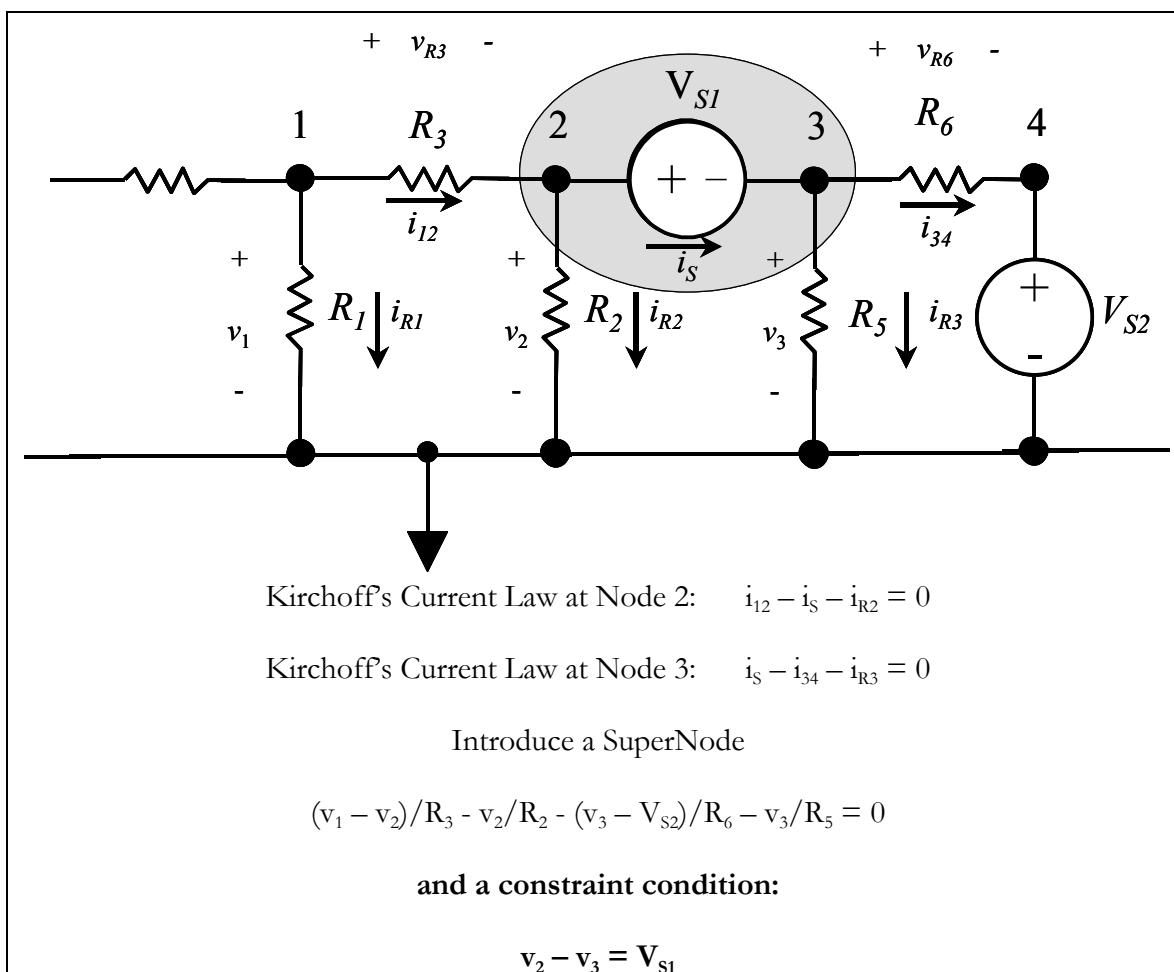We will proceed to use the equation derived from the combination of the Node 2 and Node 3 equations along with this constraint to solve for circuit variable values.



Kirchoff's Current Law at Node 2: $i_{12} + I_S - i_{R2} = 0$

or

$$(v_1 - v_2)/R_3 + I_S - v_2/R_2 = 0$$

Now, this provides all the information needed for currents to the *left* of node 2. Since the current source *defines* the current from node 2 to node 3.

We proceed to solve this problem with the additional equations that may result due to circuit components to the *left* of node 1. We will derive equations that define v_2 and v_3 .

For example, at node 3 we will have a set of equations that are independent of those at node 2.

Kirchoff's Current Law at Node 3: $-I_S - i_{34} - i_{R5} = 0$

$$-I_S - (v_3 - V_{S2})/R_6 - v_3/R_5 = 0$$

In fact, this provides enough information to solve for v_3 directly (since I_S is known and I_S defines all current flowing from 3 to 2). This effectively *isolates* node 3 from 2 for the purposes of node voltage computation.

$$v_3 = (V_{S2} - I_S R_6) R_5 / (R_5 + R_6)$$

