
HOMEWORK ASSIGNMENT 6

HOMEWORK DUE FEBRUARY 24, 2003 BEFORE CLASS:

- | | |
|---------------------------|---|
| 1. Textbook Problem 5.6 | a) -3.1mA |
| 2. Textbook Problem 5.12 | a) -4V , b) $-2.5\text{V} \leq v_b \leq -1.3\text{V}$ |
| 3. Textbook Problem 5.20 | a) $6.4\mu\text{W}$, b) $0.4\mu\text{W}$, c) 16 |
| 4. Textbook Problem 5.27 | a) 4.2V , b) $-771\text{mV} \leq v_c \leq 1371\text{mV}$ |
| 5. Textbook Problem 5.38: | a) $v_o = -9v_g/(1+10/A)$ (b) -3.24V , c) -3.60V , d) 190
Note that this operational amplifier is non-ideal |
| 6. Textbook Problem 6.7: | a) $A_1 = 0.175\text{A}$, $A_2 = -0.125$, b) $t = 152.43\mu\text{s}$ |
| 7. PSpice Problem 2: | Solve the Textbook Design Problem 5.30 |

Check the Web Site for general update and hints on homework